



**Breadboard Timer**—Shows a 555 timer astable circuit created on a breadboard.

The original circuit diagram on which this circuit is based is shown below.

Click on the **Run** button to simulate the circuit. Once simulating you can adjust **VR1** to vary the speed at which the LEDs flash.

